

Lab 2 Midterm Report on the Kinetic Inductance Detector

Kid Workgroup

Università degli studi di Roma Sapienza

May 4, 2023



Index

① Introduction

- Kid Detector
- Our Objective

② Low Frequency Circuit

- Low-pass Filter
- Amplificator and Summing Circuit

③ RF Circuit

- Splitter and Amplifier
- Mixer

Index

1 Introduction


- Kid Detector
- Our Objective

2 Low Frequency Circuit

3 RF Circuit

SAPIENZA
UNIVERSITÀ DI ROMA

Kid Detector

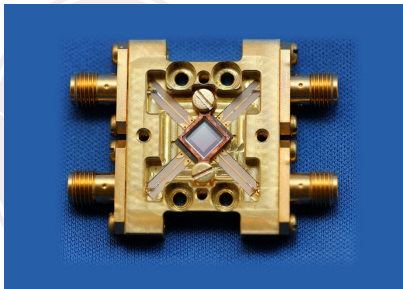


- ▶ Kinetic Inductance Detector
- ▶ Used for photon detection in a wide range of frequencies.
- ▶ Very sensible to single **photon** interaction via Cooper pairs excitation.
- ▶ Works in a **cryogenic** setting, readout via electromagnetic field variation in a **SQUID**.

Our Objective


Develop a **readout system** for the detector using an Arduino Due.

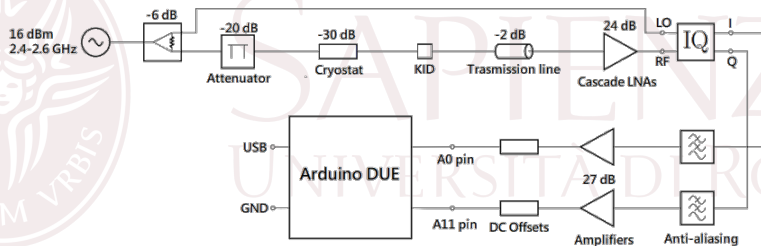The full read-out chain is comprised of an RF circuit operating at **GHz range** frequencies and an analog amplifying **anti-aliasing** circuit.



The readout works by comparing a reference signal to the signal coming out of the detector. This method is known as **homodyne detection**.

Index

- 
- 1 Introduction
 - 2 Low Frequency Circuit
 - Low-pass Filter
 - Amplificator and Summing Circuit
 - 3 RF Circuit

Low Frequency Circuit


The Low-frequency circuit serves both as an **Amplifier** and a **Anti-aliasing** filter. It has two identical channels corresponding to the I and Q signal outputted by the RF part of the readout system.

Each channel is equipped with a **3rd order Sallen key filter**, a **27dB non inverting amplifier** and a **summing circuit**.


The whole layout has been soldered on a prototype board and has BNC input.

Low-pass Filter

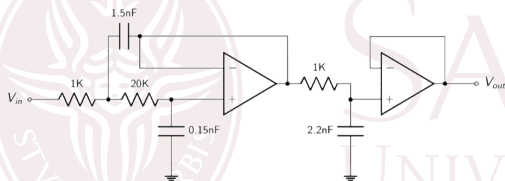The low pass filter functions as an **anti-aliasing** measure. The **sampling frequency** of the Arduino Due is about **100kHz** and as such, in order to satisfy the **Nyquist** theorem's condition for the acquisition, the **cutoff** frequency has been set at around **45 kHz**.







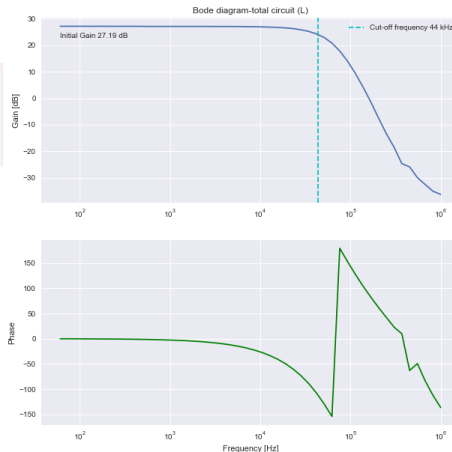Filter schematic and frequency response analysis of the whole circuit. The filter architecture is a second order **Sallen-Key** filter coupled to an **RC** filter.



Amplificator and Summing Circuit

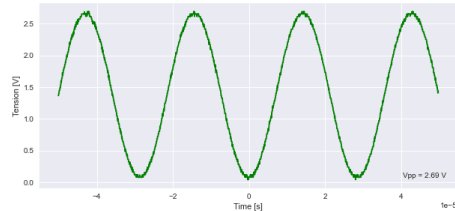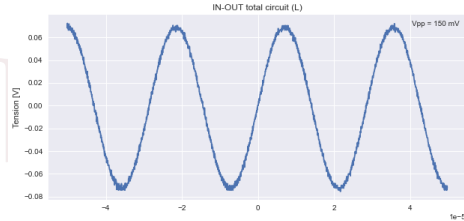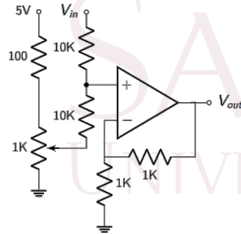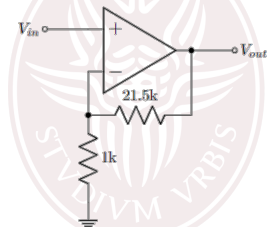In order to boost signal strength, an **amplifier** has been built. The total **gain** from amplification is **27 dB**. A **summation circuit** has been built in order to place the signal in a **range** suitable to the **Arduino (0 - 3.3 V)**.



Amplifier and summation schematic.
On the right an example of signal boosting and voltage offsetting.

Index

- 
- 1 Introduction
 - 2 Low Frequency Circuit
 - 3 RF Circuit**
 - Splitter and Amplifier
 - Mixer

SAPIENZA
UNIVERSITÀ DI ROMA

RF Circuit

The RF circuit is the part of the DAQ module directly in contact with the experimental apparatus. It's comprised of many different components connected via **SMA cables**. Each component (even the cables) has an **inherent frequency response** that must be factored in when acquiring data.


All of the apparatus works by sending a **reference signal** to the detector and the **mixer** via a **splitter**. The mixer then compares the signal from the KID and the reference one and emits the **output** to the **low-frequency circuit**.

The **KID** has an **inherent attenuation** of **30dB** and its signal must be **amplified** before it enters the mixer.

Splitter and Amplifier

The **splitter** is a component that **splits** a **signal** in two identical channels, each one carrying half the original power. We have determined, using a **Virtual Network Analyzer (VNA)**, an inherent **6 dB attenuation** due to non-ideal behavior. The **amplifier** is used to **boost** the **attenuated signal** coming from the **cryostat**, we have determined a **gain** of around **21 dB** at the desired range of frequencies.

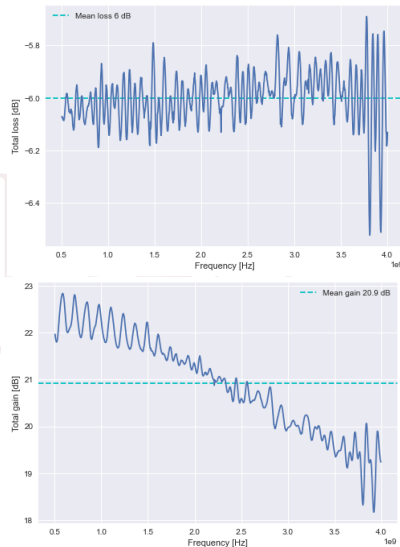Above on the right, the FRA of one of the splitter outputs. Below on the right, the FRA of the RF amplifier.



Mixer

The **Mixer** is a **non linear component**, which has an input two signals. The mixer **outputs** a signal that has as amplitude the multiplied amplitudes of the input signals times, respectively, the cos and sin of the phase difference.

It produces **two outputs**, named **I** and **Q** channel.




We have successfully **simulated DAQ** system by substituting the **cryostat** with a **20 dB attenuator** and a **2,5 meter line**.

The **two signals** should have a **90° phase difference** which was observed by measuring and plotting the **I amplitude vs the Q amplitude**.

A data taking using the Arduino has also been performed but will not be shown as we still are trying to reduce noise on this sampling method.

The **data shown** on the next slide has been **acquired** through the use of an **oscilloscope** both at the **output** of the **mixer** and the **output** of the whole **DAQ assembly**.

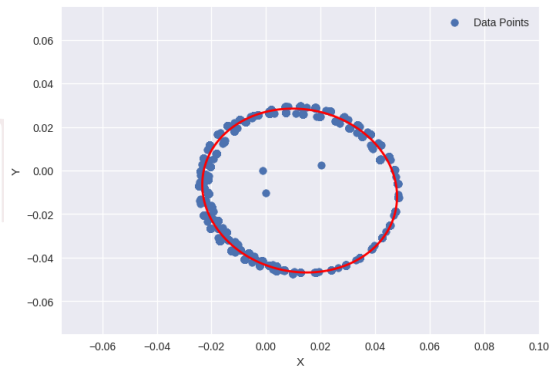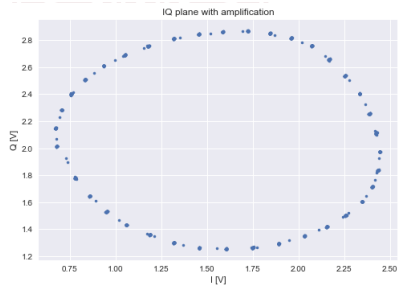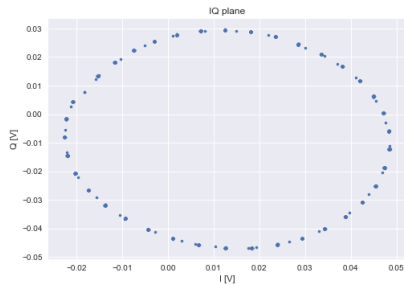The **data** taken directly from the **mixer** has then been **fitted** using an **elliptical prior**, showing an **eccentricity of 0.33**.





Thank you for your attention!

SAPIENZA
UNIVERSITÀ DI ROMA